

FPGA Design

Part VI - Advanced Topics

Thomas Lenzi

High-Speed Design Considerations

Primitives

- It is possible to implement entities that represent the building blocks of the FPGA.
- Those entities are called Primitives.
- Each FPGA family has its own set of primitives which are listed in user guides.
- Using primitives can be useful in certain cases when a specific function is needed (clock multiplexing, ...) or when you want to optimise your design beyond what ISE does.

```
and_inst: lut2_1
generic map(init => "1000")
port map(
    i0 => c(i),
    i1 => d(i),
    lo => out_and(i)
);
```

Propagation Delays


- Every component in the FPGA adds delay to the signal propagation.
- If you are working at high speed, the delay between the entry and exit point of your logic should be shorter than the period of the clock.
- If this is not the case, you will encounter undefined behaviour.

Smaller Logic

- To run at high speed, you need to break down your logic.
- Instead of comparing two 32 bits numbers in one clock cycle, which requires $11+2+1$ LUTs (cascaded), you could spread the comparison over three clock cycles.

Buffering

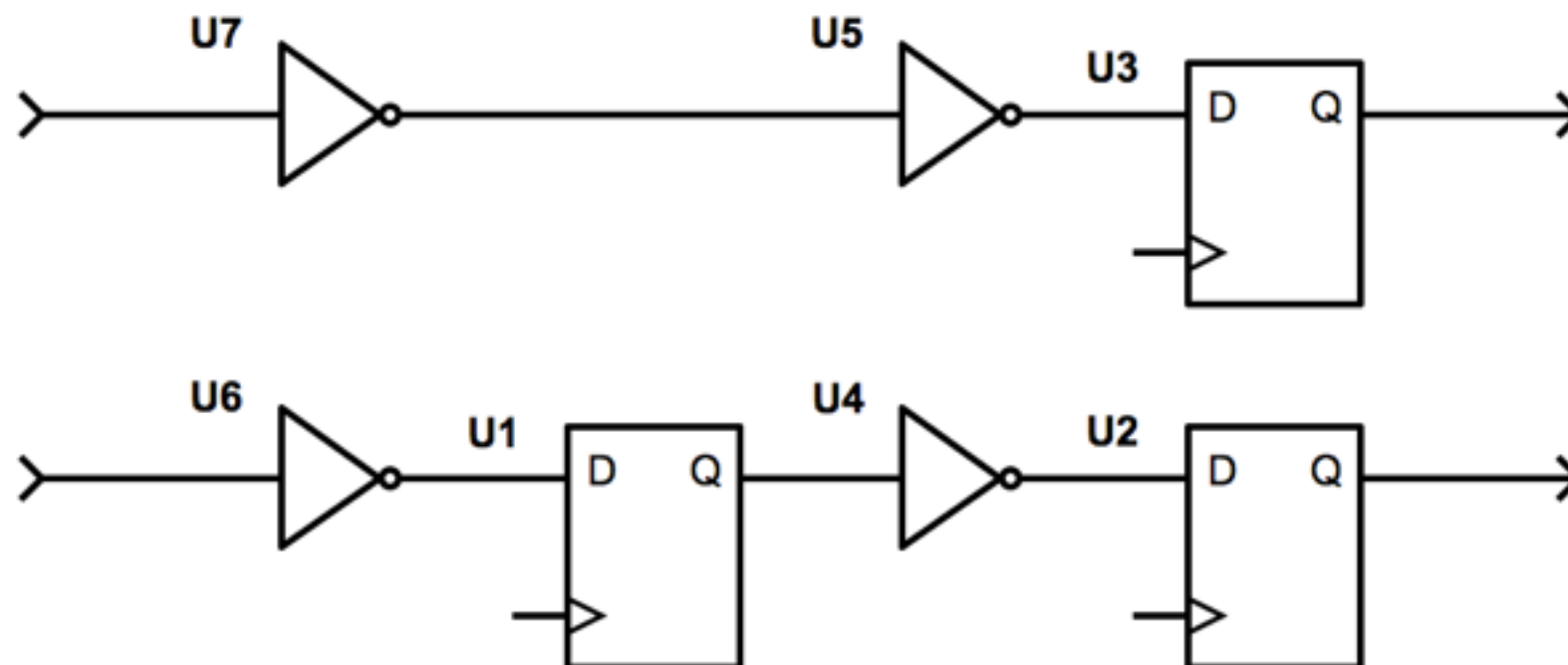- Insert DFFs in the logic to allow for faster clock speeds.
- If each inverter adds a delay of 5 ns to the logic, your clock will only be able to run at a period of 10 ns in the first case, while it can run at a period of 5 ns in the second one.



Example: 2x8bits comparator

- Stage 1:
5 LUTs, 1 DFF

```
process(clk)
begin
    if (rising_edge(clk)) then
        if (a = b) then
            dout <= '1';
        else
            dout <= '0';
        end if;
    end if;
end process;
```


Timing summary:

Timing errors: 0 Score: 0 (Setup/Max: 0, Hold: 0)

Constraints cover 0 paths, 0 nets, and 0 connections

Design statistics:

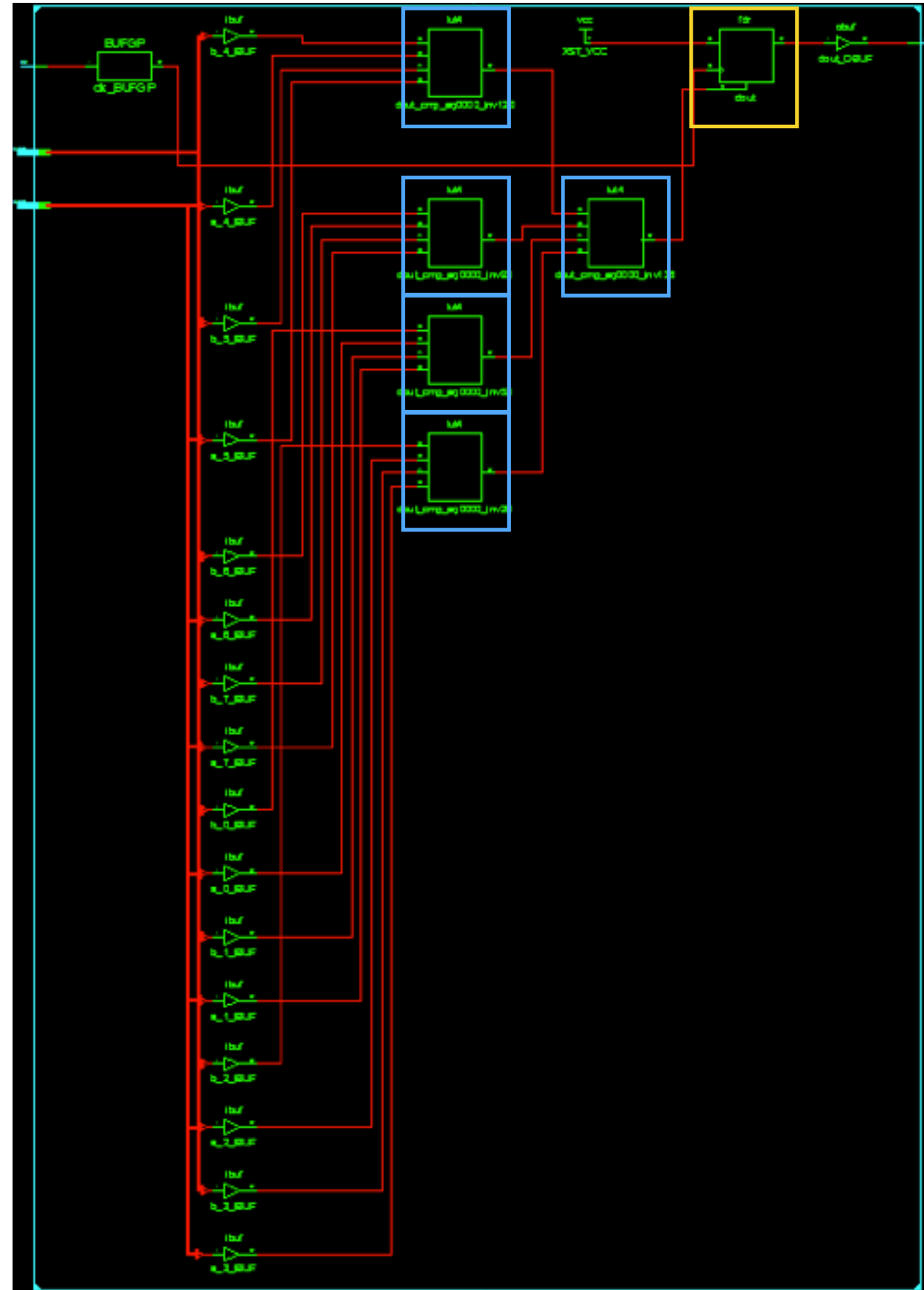Minimum period: 3.192ns(1) (Maximum frequency: 313.283MHz)



Example: 2x8bits comparator

- Stage 1:
4 LUTs, 4 DFFs
- Stage 2:
1 LUT, 1 DFF

```
-- Stage 1
stage1a_lut : lut4
generic map(init => x"9009")
port map(i0 => a(0), i1 => b(0), i2 => a(1), i3 => b(1), o => stage_1(0));

stage1b_lut : lut4
generic map(init => x"9009")
port map(i0 => a(2), i1 => b(2), i2 => a(3), i3 => b(3), o => stage_1(1));

stage1d_buf : fdce
generic map(init => '0')
port map(C => clk, D => stage_1(3), Q => stage_1_buf(3), CE => '1', CLR => '0');
```


Timing summary:

Timing errors: 0 Score: 0 (Setup/Max: 0, Hold: 0)


Constraints cover 0 paths, 0 nets, and 0 connections

Design statistics:

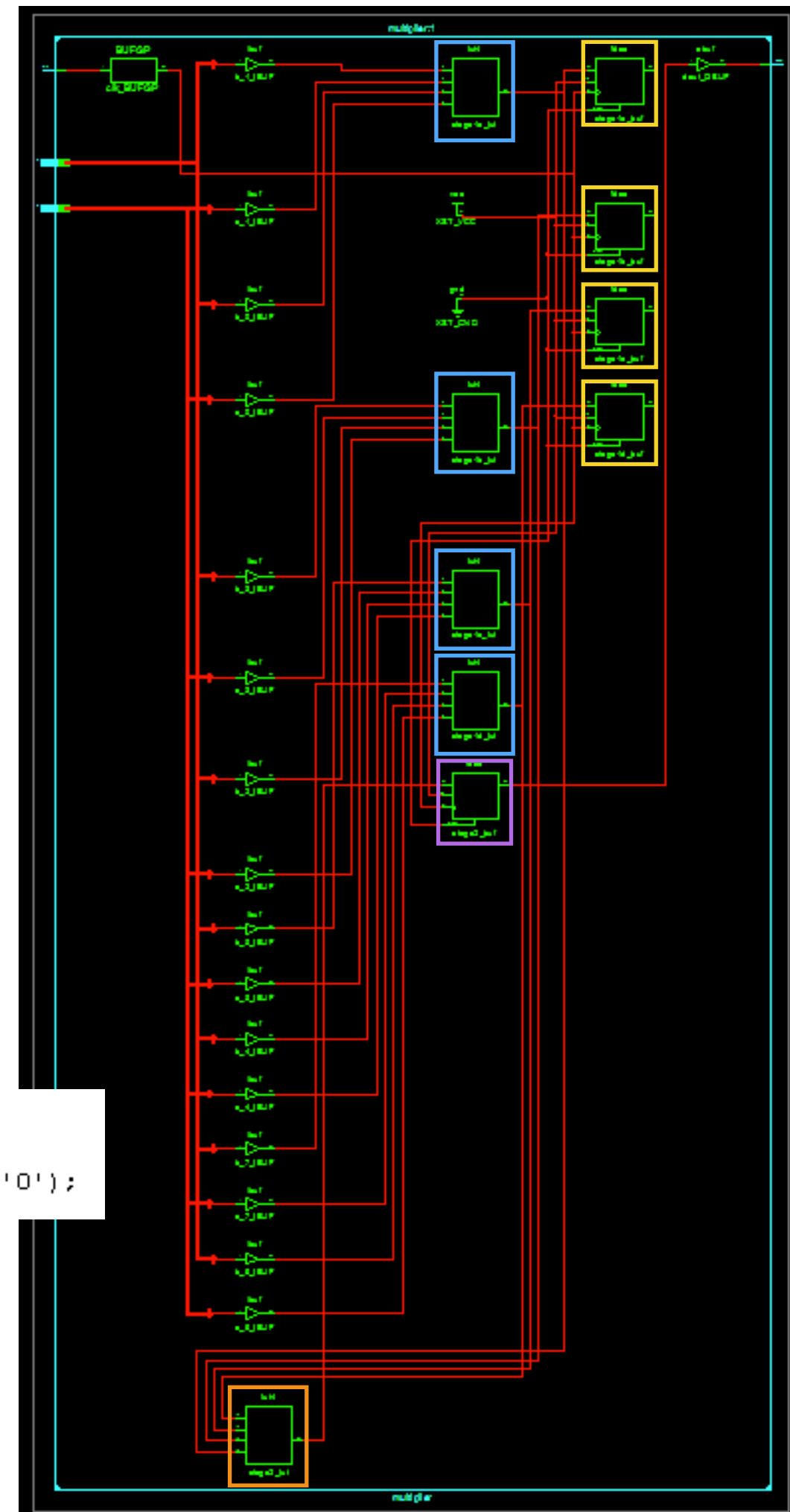Minimum period: 1.596ns{1} (Maximum frequency: 626.566MHz)



Pipelining

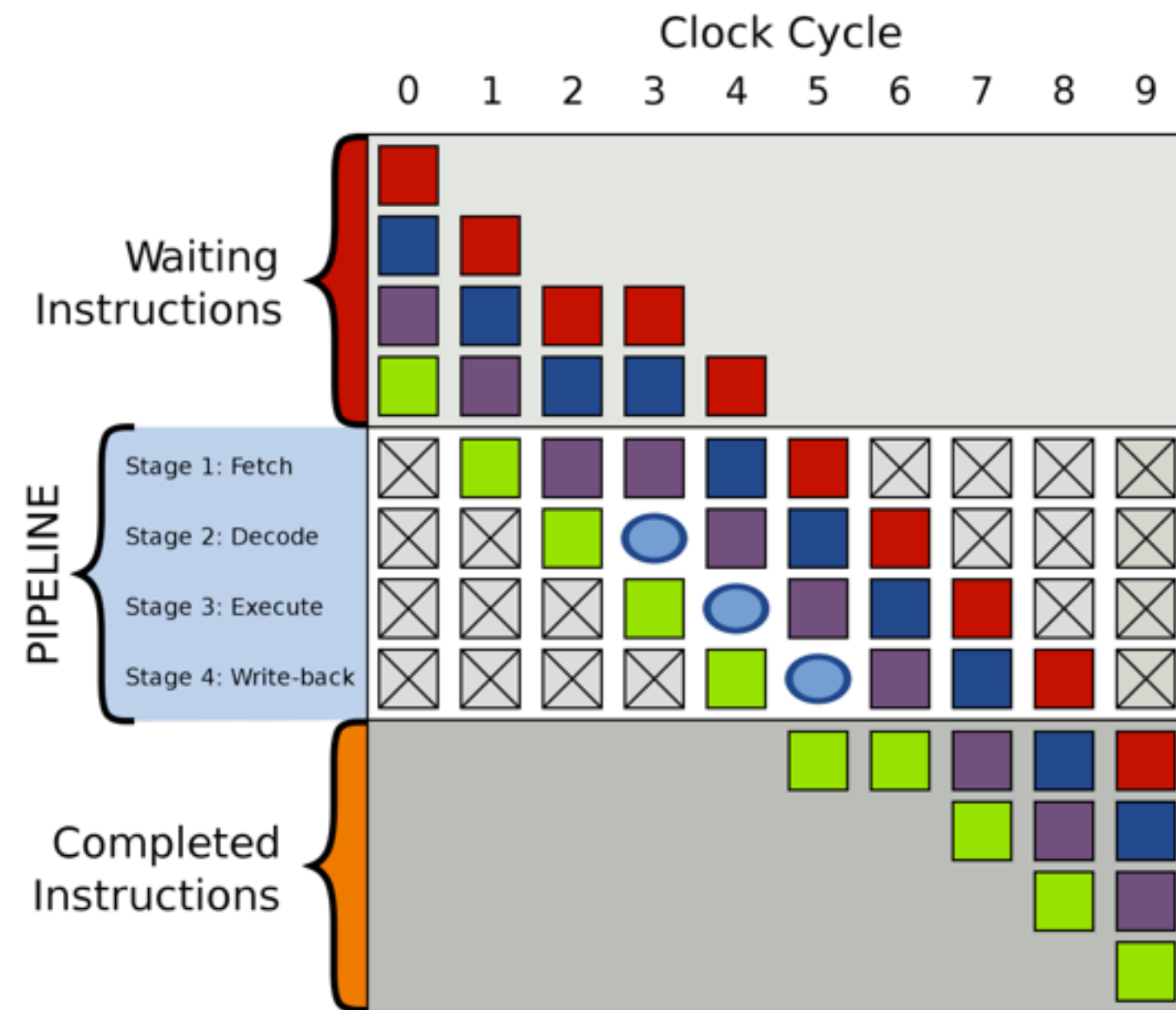


- Splitting your processes in multiple tasks doesn't mean your code will run less efficiently.
- You can for example implement pipelining, which allow two events to be processes at the same time by your machine.

How to Pipeline

- Do not make a blocking state machine in which only one event can be processed.
- Transitions between states should be done at each clock cycle so that events can follow one another.
- One *process* per action can help you visualise the workflow.
- Process data even if the input data is not valid. Let the machine run.
- Use a flag that is carried along the pipeline to indicate if the data is valid.

Multiplexing

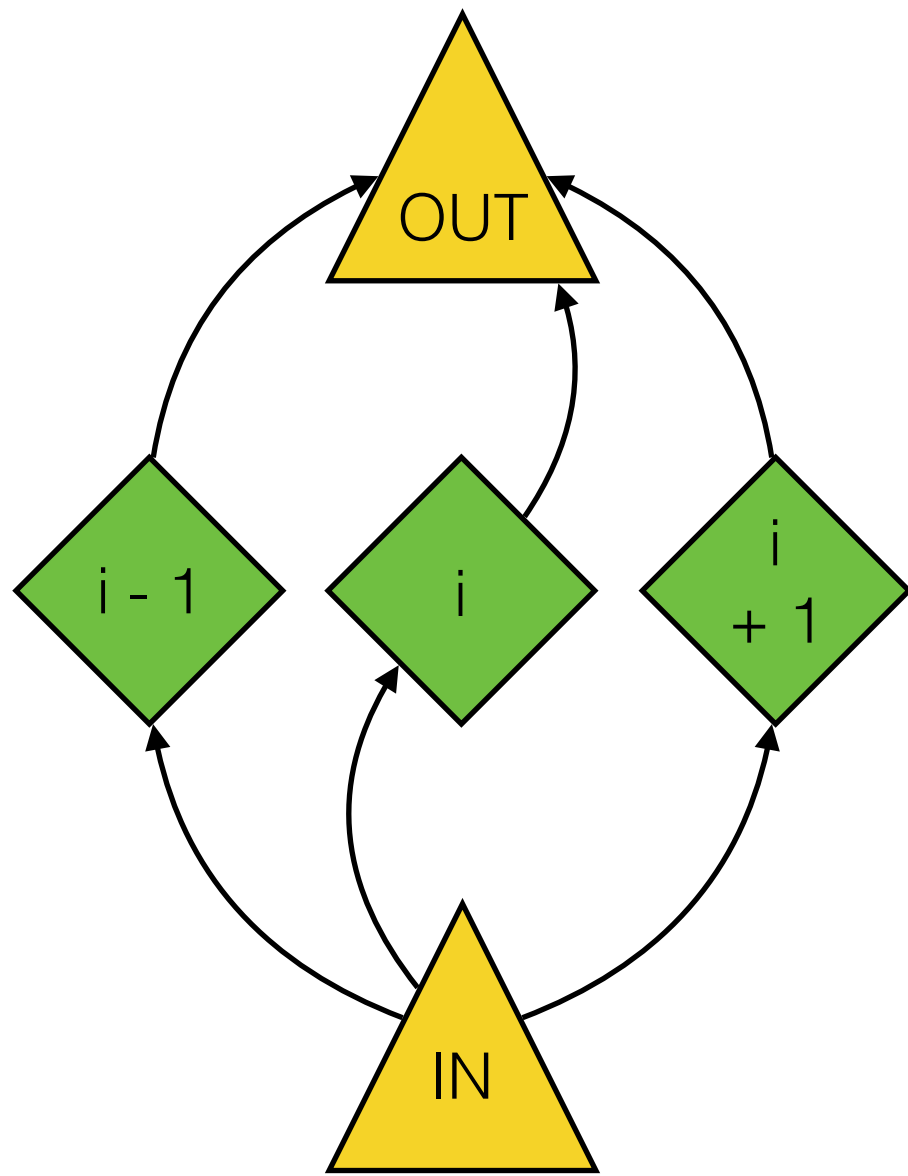

- If pipelining is not an option (task too complex to breakdown), you can consider multiplexing.
- In multiplexing, a system is duplicated N times (N is related to the execution time of the process). At each cycle, a different system is fed with information.

Timing Analysis

Timing Constraints

- You can set constraints on the clock's period in a UCF file.
- The tools will translate the design so that they can match the constraints. If the constraints cannot be match, an error occurs.

```
NET "clk" TNM_NET = "clk";  
TIMESPEC TS_clk = PERIOD "clk" 20 ns;
```

Timing Report

- ISE can generate timing reports that analyse your logic and give you information about the delays, skews, ...
- To start a timing analysis, go to “Tools > Timing Analyser > Post Place & Route...”. This option will take into account the path’s delay. The “Post Map” option will only compute the components delay.

Floorplanning

Floorplanning

- Floorplanning allows you to define regions of the FPGA in which the Xilinx tools should place certain components.
- You can even go as far as placing the LUTs, DFFs, ... manually.

Hierarchical Design

- When synthesising your design, you can tell ISE to keep the hierarchy of your design.
- This means that the entities will keep their name and be easier to place on the FPGA. You will be able to place certain components in given regions.

Problem

```
entity challenge is
port(
    clk          : in std_logic;
    a            : in std_logic_vector(7 downto 0);
    b            : in std_logic_vector(7 downto 0);
    c            : in std_logic_vector(3 downto 0);
    d            : in std_logic_vector(3 downto 0);
    e            : out std_logic_vector(3 downto 0)
);
end challenge;

architecture behavioral of challenge is

begin

    process(clk)
    begin
        if (rising_edge(clk)) then
            if (unsigned(a) = unsigned(b)) then
                e <= c or d;
            else
                e <= c and d;
            end if;
        end if;
    end process;

end behavioral;
```

- Optimise the logic shown on the left for area by placing the components manually.
- You should first translate it to building blocks.

Ressources

- View of CLB at page 22: http://www.xilinx.com/support/documentation/data_sheets/ds312.pdf
- Primitives: http://www.xilinx.com/support/documentation/sw_manuale/xilinx12_4/spartan3e_hdl.pdf
- UCF to use: <http://iihe.ac.be/~tlenzi/challenge.ucf>